Міністерство освіти і науки України

Національний університет "Львівська політехніка"

Кафедра ЕОМ



3 лабораторної роботи №3

3 дисципліни: «Моделювання комп'ютерних систем»

На тему: «Поведінковий опис цифрового автомата. Перевірка роботи автомата за допомогою стенда Elbert V2 – Spartan 3A FPGA»

Варіант-7

Виконав:

Душний О.І.

Прийняв:

Козак Н.Б


Мета: На базі стенда Elbert V2 – Spartan 3A FPGA реалізувати цифровий автомат для обчислення виразу.

Завдання

На базі стенда реалізувати цифровий автомат для обчислення значення виразу дотримуючись наступних вимог:

1) Функціонал пристрою повинен бути реалізований згідно отриманого варіанту завдання:

 2) Пристрій повинен бути ітераційним АЛП повинен виконувати за один такт одну операцію та реалізованим згідно наступної структурної схеми:



Хід роботи

1. Створю файл Mux.vhd в якому реалізовую мультиплексор:

```
entity MUX is
    Port ( DATA IN : in STD LOGIC VECTOR (7 downto 0);
            RAM_IN : in STD_LOGIC_VECTOR (7 downto 0);
IN_SEL : in STD_LOGIC_VECTOR (1 downto 0);
            MUX DATA OUT : OUT STD LOGIC VECTOR (7 downto 0));
end MUX;
architecture Behavioral of MUX is
begin
    process(DATA IN, IN SEL, RAM IN)
    begin
      if (IN SEL = "00") then
         MUX DATA OUT <= DATA IN;
      elsif(IN SEL = "01") then
         MUX DATA OUT <= RAM IN;
      elsif(IN SEL = "10")then
         MUX DATA OUT <= "00000101";
         MUX DATA OUT <= "000000000";
      end if;
    end process;
end Behavioral;
```

2. Створюю файл ACC.vhd, в якому реалізовую регістр:

```
entity ACC is
    Port ( INPUT BUS : in STD LOGIC VECTOR (7 downto 0);
           OUTPUT BUS : out STD LOGIC VECTOR (7 downto 0);
          ACC WR : in STD LOGIC;
          ACC RST : in STD LOGIC;
           CLOCK : in STD LOGIC);
end ACC;
architecture Behavioral of ACC is
signal ACC DATA : STD LOGIC VECTOR (7 downto 0);
begin
process (CLOCK, INPUT BUS, ACC DATA)
    begin
      if (rising edge(CLOCK)) then
         if (ACC RST = '1') then
            ACC DATA <= "000000000";
         elsif (ACC WR = '1') then
           ACC DATA <= INPUT BUS;
         end if;
      end if;
      OUTPUT BUS <= ACC DATA;
    end process;
end Behavioral;
```

3. Створюю файл ALU.vhd, який реалізовує арифметико-логічний пристрій, що підтримує операції, необхідні для виконання виразу згідно з варіантом, а саме операції: «+», «-» та «SLL»:

```
entity ALU is
   Port ( A BUS : in STD_LOGIC_VECTOR (7 downto 0);
B BUS : in STD_LOGIC_VECTOR (7 downto 0);
          OUT_BUS : out STD_LOGIC_VECTOR (7 downto 0);
OP_CODE : in STD_LOGIC_VECTOR (1 downto 0);
OVERFLOW : out STD_LOGIC);
end ALU;
architecture Behavioral of ALU is
process(OP_CODE, A_BUS, B_BUS)
     variable A : unsigned(7 downto 0);
      variable B : unsigned(7 downto 0);
        A := unsigned(A_BUS);
        B := unsigned(B_BUS);
       case(OP_CODE) is
           when "00" =>
              OUT_BUS <= STD_LOGIC_VECTOR(B);
              OVERPLOW <= '0';
           when "01" =>
          if ((A > 128 and B > 127) or (A > 127 and B > 128)) then
               OVERFLOW <= '1';
              OVERPLOW <= '0';
          end if;
               OUT_BUS <= STD_LOGIC_VECTOR(A - B);
            when "10" =>
           if (A < B) then
               OVERFLOW <= '1';
               OVERFLOW <= '0';
           end if;
              OUT_BUS <= STD_LOGIC_VECTOR(A + B);
          when "11" =>
               OUT_BUS <= STD_LOGIC_VECTOR(A s11 2);
              OVERFLOW <= '0':
           when others =>
              OUT BUS <= "000000000";
               OVERFLOW <= '0';
        end case;
    end process;
end Behavioral;
```

4. Визначивши множину станів та умови переходу пристрою керування (CU), необхідних для обчислення виразу, створюю новий файл CU.vhd, який реалізовує пристрій керування, згідно визначеного алгоритму:

```
entity CU is
    Port (ENTER_OP1 : in STD_LOGIC;

ENTER_OP2 : in STD_LOGIC;

CALCULATE : in STD_LOGIC;

RESET : in STD_LOGIC;

RAM_WR : out STD_LOGIC;
               RAM ADDR BUS : out STD_LOGIC_VECTOR (1 downto 0);
              ACC_WR : out STD_LOGIC;
ACC_RST : out STD_LOGIC;
IN_SEL : out STD_LOGIC_VECTOR (1 downto 0);
OP_CODE_BUS : out STD_LOGIC_VECTOR (1 downto 0);
CLOCK : IN_STD_LOGIC_VECTOR (1 downto 0);
end CU;
architecture CU_arch of CU is
type cu_state_type is (cu_rst, cu_idle, cu_load_opl, cu_load_op2, cu_rum_calc0, cu_rum_calc1, cu_rum_calc2, cu_rum_calc2, cu_finish);
signal cu_cur_state : cu_state_type;
signal cu_next_state : cu_state_type;
begin
   process (CLOCK)
    begin
       if (rising_edge(CLOCK)) then
if (RESET = '1') then
                cu_cur_state <= cu_rst;
               cu_cur_state <= cu_next_state;
           end if;
        end if:
    end process;
    process (cu_cur_state, ENTER_OP1, ENTER_OP2, CALCULATE)
    begin
       --declare default state for next_state to avoid latches
cu_next_state <= cu_cur_state: --default is to stay in current state
        --insert statements to decode next_state
       --below is a simple example
```

```
case(cu_cur_state) is
        when cu_rst =>
           cu_next_state <= cu_idle:
        when cu idle =>
           if (ENTER_OP1 = '1') then
             cu_next_state <= cu_load_opl;
           elsif (ENTER_OP2 = '1') then
             cu_next_state <= cu_load_op2;
           elsif (CALCULATE = '1') then
             cu_next_state <= cu_run_calc0;
           else
             cu_next_state <= cu_idle;
           end if:
        when cu_load_opl =>
           cu_next_state <= cu_idle;
        when cu_load_op2 =>
           cu_next_state <= cu_idle;
        when cu_run_calc0 =>
           cu_next_state <= cu_run_calcl;
        when cu_run_calc1 =>
           cu_next_state <= cu_run_calc2;
        when cu_run_calc2 =>
           cu_next_state <= cu_run_calc3;
        when cu_run_calc3 =>
           cu_next_state <= cu_finish;
        when cu_finish =>
           cu_next_state <= cu_finish;
        when others =>
          cu_next_state <= cu_idle;
     end case;
   end process;
process (cu_cur_state)
  begin
     case(cu_cur_state) is
        when cu_rst =>
IN_SEL <= "00";
           OP_CODE_BUS <= "00";
RAM_ADDR_BUS <= "00";
           RAM_WR <= '0';
           ACC_RST
                         <= '1';
                        <= '0';
          ACC_WR
        when cu_idle =>
                         <= "00";
           IN_SEL
                         <= "00";
           OP_CODE_BUS
           RAM_ADDR_BUS <= "00";
                         <= '0';
          RAM_WR
           ACC RST
                        <= '0';
                         <= '0';
           ACC_WR
        when cu_load_opl =>
           IN_SEL
                         <= "00";
           OP_CODE_BUS <= "00";
           RAM_ADDR_BUS <= "00";
                         <= '1';
           RAM WR
           ACC_RST
                         <= '0';
           ACC_WR
                         <= '1';
        when cu_load_op2 =>
                         <= "00";
           IN SEL
                         <= "00";
           OP_CODE_BUS
           RAM_ADDR_BUS <= "01";
           RAM_WR <= '1';
ACC_RST <= '0';
                                                                    end CU_arch;
           ACC_WR
                      <= 'l';
```

```
when cu_run_calc0 =>
       IN_SEL <= "01";
OP_CODE_BUS <= "00";
       RAM_ADDR_BUS <= "00";
                    <= '0';
       RAM_WR
                     <= '0':
       ACC_RST
       ACC_WR
                    <= '1';
     when cu_run_calc1 =>
                     <= "00";
       IN SEL
                     <= "11";
       OP_CODE_BUS
       RAM_ADDR_BUS <= "01";
                 <= '0';
       RAM_WR
       ACC_RST
                     <= '0';
                     <= '1';
       ACC_WR
     when cu_run_calc2 =>
                   <= "01";
       IN_SEL
       OP_CODE_BUS
                     <= "01";
       RAM_ADDR_BUS <= "01";
                    <= '0';
       RAM WR
                    <= '0';
       ACC_WR
       ACC_RST
                    <= '1';
     when cu_run_calc3 =>
                   <= "10";
       IN SEL
       OP_CODE_BUS
                     e= "10";
       RAM_ADDR_BUS <= "00";
               <= '0';
       RAM_WR
       ACC_RST
                     <= '0';
       ACC_WR
                     <= '1';
     when cu_finish =>
                     <= "00";
       IN_SEL
       OP_CODE_BUS
                     <= "00";
       RAM_ADDR_BUS <= "00";
                     <= '0';
       RAM_WR
       ACC_RST
                     <= '0';
       ACC_WR
                    <= '0';
     when others =>
                    <= "00";
       IN_SEL
       OP_CODE_BUS
                     <= "00";
       RAM_ADDR_BUS <= "00";
                    <= '0';
       RAM_WR
       ACC_RST
                     <= '0';
                     <= '0';
       ACC_WR
  end case;
end process;
```

5. Створюю файл RAM.vhd, в якому реалізовую пам'ять пристрою:

```
entity RAM is
   Port ( DATA : in STD LOGIC VECTOR (7 downto 0);
          RAM ADDR : in STD LOGIC VECTOR (1 downto 0);
          RAM WR : in STD LOGIC;
          CLOCK : in STD LOGIC;
          OUT DATA : out STD LOGIC VECTOR (7 downto 0));
end RAM;
architecture Behavioral of RAM is
type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7 downto 0);
signal RAM_UNIT : ram_type;
begin
   process(CLOCK, RAM ADDR, RAM UNIT)
     if (rising edge(CLOCK)) then
        if (RAM WR = '1') then
          RAM UNIT (conv integer (RAM ADDR)) <= DATA;
       end if;
     end if;
     OUT_DATA <= RAM_UNIT(conv_integer(RAM_ADDR));
   end process;
end Behavioral;
```

6. Створюю файл Indicator.vhd, в якому реалізовую блок індикації (7-SEG DECODER):

```
entity HEX_DECODER is
     Port ( DATA_IN : in STD_LOGIC_VECTOR (7 downto 0);
               CLOCK : in STD_LOGIC;
               CLOCK: In SID_LOGIC;

RESET: in STD_LOGIC;

SEG_DATA: out SID_LOGIC VECTOR (7 downto 0) := "10000000";


COMM_ONES: OUT SID_LOGIC := '0';

COMM_DECS: OUT SID_LOGIC := '0';


COMM_HUNDREDS: OUT SID_LOGIC := '0');
end HEX DECODER;
architecture Behavioral of HEX DECODER is
signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "00001";
signal HUNDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "00000";
     process (DATA IN)
          variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
variable bcd : STD_LOGIC_VECTOR(11 downto 0) ;
     begin
          bcd := (others => '0') ;
hex_src := DATA_IN;
          for i in hex src'range loop
               if bcd(3 downto 0) > "0100" then
                     bcd(3 downto 0) := bcd(3 downto 0) + "0011";
                end if ;
                if bcd(7 downto 4) > "0100" then
                    bcd(7 downto 4) := bcd(7 downto 4) + "0011";
                end if ;
                if bcd(l1 downto 8) > "0100" then
                     bcd(11 downto 8) := bcd(11 downto 8) + "0011";
                bcd := bcd(10 downto 0) & hex src(hex src'left) ; -- shift bcd + 1 new entry
                hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; -- shift src + pad with 0
           end loop ;
          HUNDREDS_BUS <= bcd (11 downto 8);
DECS_BUS <= bcd (7 downto 4);
ONES_BUS <= bcd (3 downto 0);
     end process;
     process (CLOCK)
        type DIGIT TYPE is (ONES, DECS, HUNDREDS);
```

```
variable CUR_DIGIT : DIGIT_TYPE := ONES;
variable DIGIT_VAL : STD_LOGIC_VECTOR(2 downto 0) := "00000";
variable DIGIT_CTRL : STD_LOGIC_VECTOR(6 downto 0) := "0000000";
      variable COMMONS_CTRL : STD_LOGIC_VECTOR(2 downto 0) := "000";
         if (rising_edge(CLOCK)) then
            if(RESET = '0') then
                case CUR_DIGIT is
                  when ONES =>
                         DIGIT VAL := ONES BUS;
                         CUR DIGIT := DECS;
                         COMMONS_CTRL := "001";
                   when DECS =>
                        DIGIT VAL := DECS BUS;
                         CUR_DIGIT := HUNDREDS;
                         COMMONS_CTRL := "010";
                   when HUNDREDS =>
                         DIGIT_VAL := HUNDREDS_BUS;
                         CUR DIGIT := ONES;
                         COMMONS_CTRL := "100";
                   when others =>
                         DIGIT_VAL := ONES_BUS;
                         CUR_DIGIT := ONES;
                         COMMONS_CTRL := "000";
               end case;
                case DIGIT_VAL is
                   when "0000" => DIGIT_CTRL := "1111110";
when "0001" => DIGIT_CTRL := "0110000";
                   when "0010" => DIGIT_CTRL := "1101101";
                   when "0011" => DIGIT_CTRL := "1111001";
                   when "0100" => DIGIT_CTRL := "0110011";
                   when "0101" => DIGIT CTRL := "1011011";
                   when "0110" => DIGIT CTRL := "1011111";
                   when "0111" => DIGIT_CTRL := "1110000";
                   when "1000" => DIGIT_CTRL := "11111111";
                   when "1001" => DIGIT_CTRL := "1111011";
                   when others => DIGIT_CTRL := "0000000";
                end case;
             else
                DIGIT_VAL := ONES_BUS;
                CUR_DIGIT := ONES;
                COMMONS_CTRL := "000";
            end if:
         COMM_ONES <= COMMONS_CTRL(0);
COMM_DECS <= COMMONS_CTRL(1);
         COMM_HUNDREDS <= COMMONS_CTRL(2);
         SEG_DATA(6) <= (DIGIT_CTRL(6) mor '1');
          SEG_DATA(5) <= (DIGIT_CTRL(5) nor '1');
         SEG_DATA(4) <= (DIGIT_CTRL(4) nor '1');
          SEG_DATA(2) <= (DIGIT_CTRL(2) mor '1');
         SEG_DATA(2) <= (DIGIT_CTRL(2) mor '1');
          SEG_DATA(1) <= (DIGIT_CTRL(1) mor '1');</pre>
         SEG_DATA(0) <= (DIGIT_CTRL(0) nor '1');
         -- SEG_DATA(7) <= '0';
         end if:
   end process;
end Behavioral;
```

 7. Згенерувавши символи для раніше імплементованих компонентів створюю файл верхнього рівня TopLevel.sch, в якому виконую інтеграцію компонентів системи між собою та зі стендом Elbert V2 – Spartan 3A FPGA:



 8. За допомогою симулятора ISim симулюю роботу пристрою:



9. Призначив виводам схеми фізичні виводи цільової FPGA

```
LOC - P117 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
    NET "SEG DATA[6]"
                          LOC - P116 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
    NET "SEG DATA[5]"
    NET "SEG DATA[4]"
                         LOC - P115 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
                        LOC - P113 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
    NET "SEC DATA(3)"
    NET "SEC DATA121"
                         LOC - P112 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
                        LOC - P111 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
LOC - P110 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
LOC - P114 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
    NET "SEG DATA[1]"
    NET "SEC DATA[0]"
    NET "SEG DATAITI"
    NET "COMM BUNDREDS"
                              LOC - P124 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
    NET "COMM DECS"
                              LOC - P121 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
    NET "COMM ONES"
                              LOC - P120 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
LED
NET "OVERPLOW"

LOC - P46 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
#NET "OUT BUS(1)"

LOC - P47 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
#NET "OUT BUS(2)"

LOC - P48 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
#NET "OUT BUS(3)"

LOC - P49 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
#NET "OUT BUS(4)"

LOC - P50 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
#NET "OUT BUS(5)"


LOC - P51 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
#NET "OUT BUS(6)"

LOC - P54 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
#NET "OUT BUS(7)"

LOC - P55 | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
#NET "OUT BUS(7)"
NET "DATA INIO1"
                                         | PULLUP | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 124
    NET "DATA IN[1]"
                            LOC - P69 | PULLUP | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
    NET "DATA IN[2]"
                            LOC - P68
                                         | PULLUP | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
    NET "DATA IN[3]"
                            LOC - P64 | PULLUP | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
                            LOC - P63 | PULLUP | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
LOC - P60 | PULLUP | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
LOC - P59 | PULLUP | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
    NET "DATA IN[4]"
    NET "DATA IN[5]"
    NET "DATA IN[6]"
    NET "DATA IN[7]"
                             LOC - P58 | PULLUP | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
NET "ENTER OP1"
                                 LOC - PRO | PULLUP | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12:
                                 LOC = P79 | PULLUP | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
LOC - P78 | PULLUP | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
    NET "ENTER OP2"
                                 LOC - P78
    NET "RESET"
    NET "CALCULATE"
                                               | PULLUP | IOSTANDARD - LVCMOS33 | SLEW - SLOW | DRIVE - 12;
```

Згенерував ВІТ файл для цільової FPGA.

 Послідовно запустив процеси Synthesize-XST, Implement Design та Generate Programming File:



Висновок

На цій лабораторній роботі я навчився на базі стенда Elbert V2 – Spartan 3A FPGA, реалізовувати цифровий автомат для обчислення значення виразу.